 



CSCB58: Computer Organization



Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

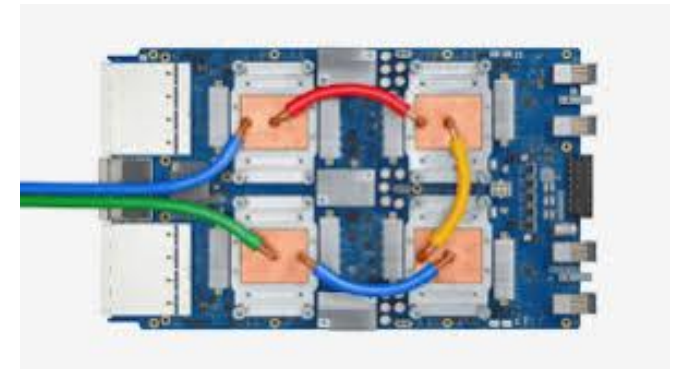


*The content of this lecture is adapted from the lectures of
Larry Zheng and Steve Engels*

CSCB58 Week 3

Quiz 1: Question 2 Clarification


Attempts: 97 out of 97

Adding impurities to the semiconductors causes (select all that apply.)

Instability in the semiconductor	71 respondents	73 %	
It to be positively/negatively charged	30 respondents	31 %	
It to have more mobile electrons/holes	86 respondents	89 %	
Increase in resistance in the semiconductor	12 respondents	12 %	

12% answered correctly

We are here

 


Logical Devices

Building up from gates...


- Some common and more complex structures:
 - Multiplexers (MUX)
 - Adders (half and full)
 - Subtractors
 - Decoders
 - Seven-segment decoders
 - Comparators

Multiplexers

 

Logical devices

 - Certain structures are common to many circuits, and have block elements of their own.
 - e.g. Multiplexers (short form: **mux**)
 - Behaviour: Output is X if S is 0, and Y if S is 1, i.e., S selects which input can go through




Multiplexer design

X	Y	S	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

	$\bar{Y} \cdot \bar{S}$	$\bar{Y} \cdot S$	$Y \cdot S$	$Y \cdot \bar{S}$
\bar{X}	0	0	1	0
X	1	0	1	1

$$M = Y \cdot S + X \cdot \bar{S}$$

 


Multiplexer uses

- Muxes are very useful whenever you need to select from multiple input values.
 - Example:
 - Surveillance video monitors,
 - Digital cable boxes,
 - routers.



Demultiplexers

 - Does multiplexer operation, in reverse.



Mux + Demux



Adder circuits



Adders

- Also known as binary adders.
 - Small circuit devices that add two **1-bit** number.
 - Combined together to create **iterative combinational circuits** – add **multiple-bit** numbers
- Types of adders:
 - Half adders (HA)
 - Full adders (FA)
 - Ripple Carry Adder
 - Carry-Look-Ahead Adder (CLA)

Review of Binary Math

Review of Binary Math

- Each digit of a decimal number represents a power of 10:

$$258 = 2 \times 10^2 + 5 \times 10^1 + 8 \times 10^0$$

- Each digit of a binary number represents a power of 2:


$$\begin{aligned} 01101_2 &= 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ &= 13_{10} \end{aligned}$$

Unsigned binary addition

• 27 + 53

27 = 00011011

53 = 00110101

 


01010000

• 95 + 181

01011111

+10110101

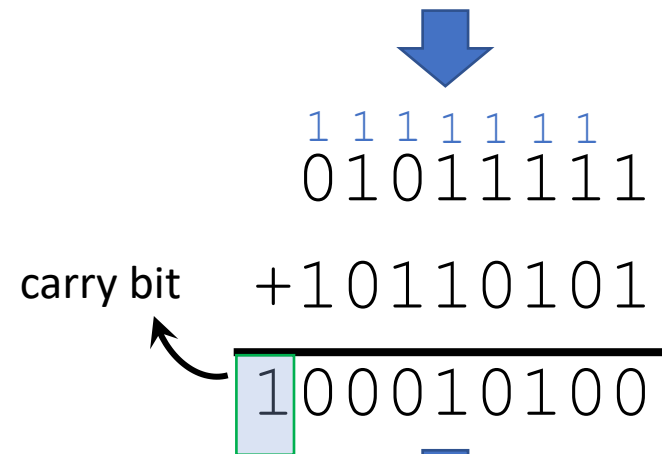

00010100

Half Adder

Input: two 1-bit numbers

Output: 1-bit sum and 1-bit carry

Half Adders


- A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
+Y	+0	+1	+0	+1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
CS	00	01	01	10

$$C = X \cdot Y$$

$$S = X \oplus Y$$

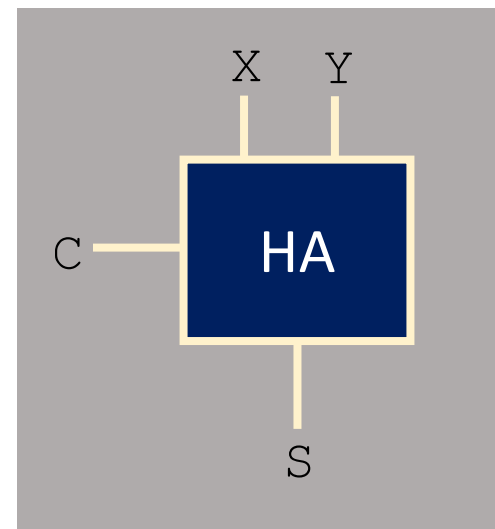
- A half adder adds two bits to produce a two-bit sum.
- The sum is expressed as a sum bit S and a carry bit C .



Half Adder Implementation

- Equations and circuits for half adder units are easy to define (even without Karnaugh maps)

 
$$C = X \cdot Y \quad S = X \cdot \bar{Y} + \bar{X} \cdot Y \\ = X \text{ xor } Y$$



A half adder **outputs** a carry-bit,
but does not take a carry-bit as **input**.


Full Adder

takes a carry bit as **input**

 

Full Adders

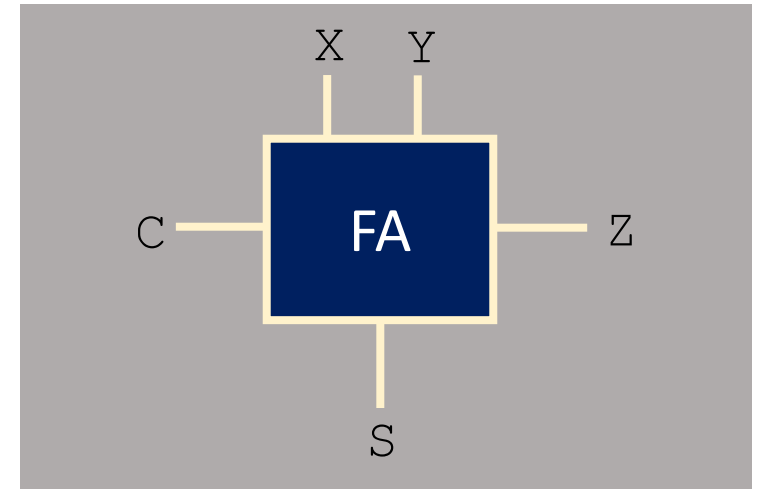- Similar to half-adders, but with another input Z , which represents a **carry-in bit**.
 - C and Z are sometimes labeled as C_{out} and C_{in} .
- When Z is 0, the unit behaves exactly like...
 - a half adder.
- When Z is 1:



X	0	0	1	1
+Y	+0	+1	+0	+1
+Z	+1	+1	+1	+1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
CS	01	10	10	11

Full Adder Design

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C	$\bar{Y} \cdot \bar{Z}$	$\bar{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \bar{Z}$
\bar{X}	0	0	1	0
X	0	1	1	1

S	$\bar{Y} \cdot \bar{Z}$	$\bar{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \bar{Z}$
\bar{X}	0	1	0	1
X	1	0	1	0

$$C = X \cdot Y + X \cdot Z + Y \cdot Z$$

$$C = X \cdot Y + (X \text{ xor } Y) \cdot Z$$

$$S = X \text{ xor } Y \text{ xor } Z$$

For gate reuse ($X \text{ xor } Y$)
considering both C and S


Full Adder Design

$$S = X \text{ xor } Y \text{ xor } Z$$

- The C term can also be rewritten as:

$$C = X \cdot Y + (X \text{ xor } Y) \cdot Z$$

 
- Two terms come from this:
 - $X \cdot Y =$ carry generate (G).
 - Whether X and Y generate a carry bit
 - $X \text{ xor } Y =$ carry propagate (P).
 - Whether carry will be propagated to Cout
- Results in this circuit →






Now we can add one bit properly, but most of the numbers we use have more than one bits.

- int, unsigned int: 32 bits (architecture-dependent)
- short int, unsigned short int: 16 bits
- long long int, unsigned long long int: 64 bit
- char, unsigned char: 8 bits

How do we add multiple-bit numbers?

 

  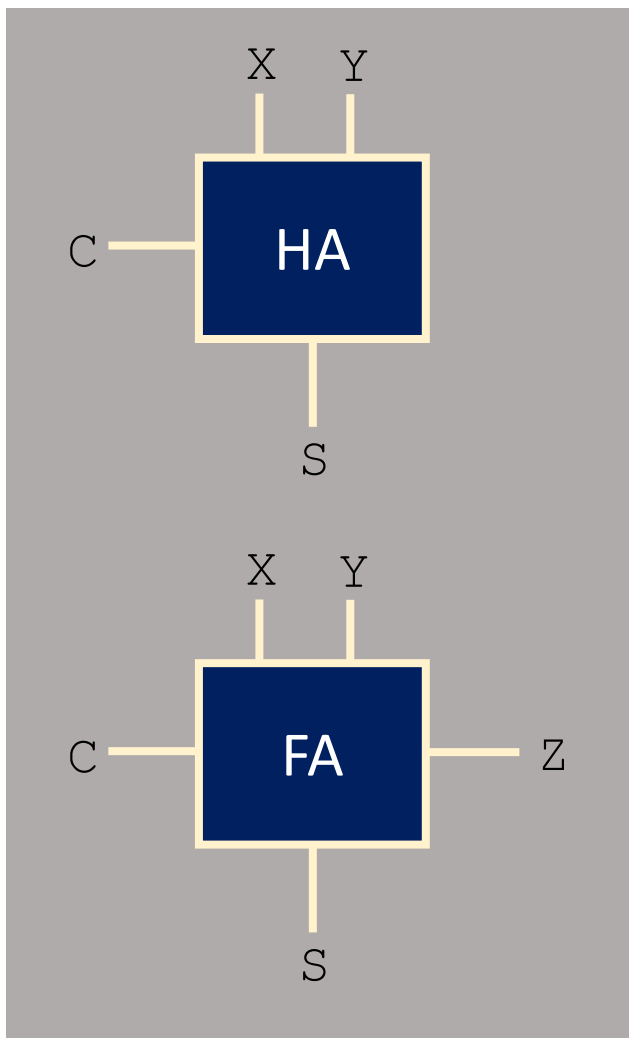

Each full adder takes in a carry bit and outputs a carry bit.

Each full adder can take in a carry bit which is output by another full adder.


That is, they can be **chained** up.

Ripple-Carry Binary Adder

Full adders chained up,
for **multiple-bit** addition

Ripple-Carry Binary Adder

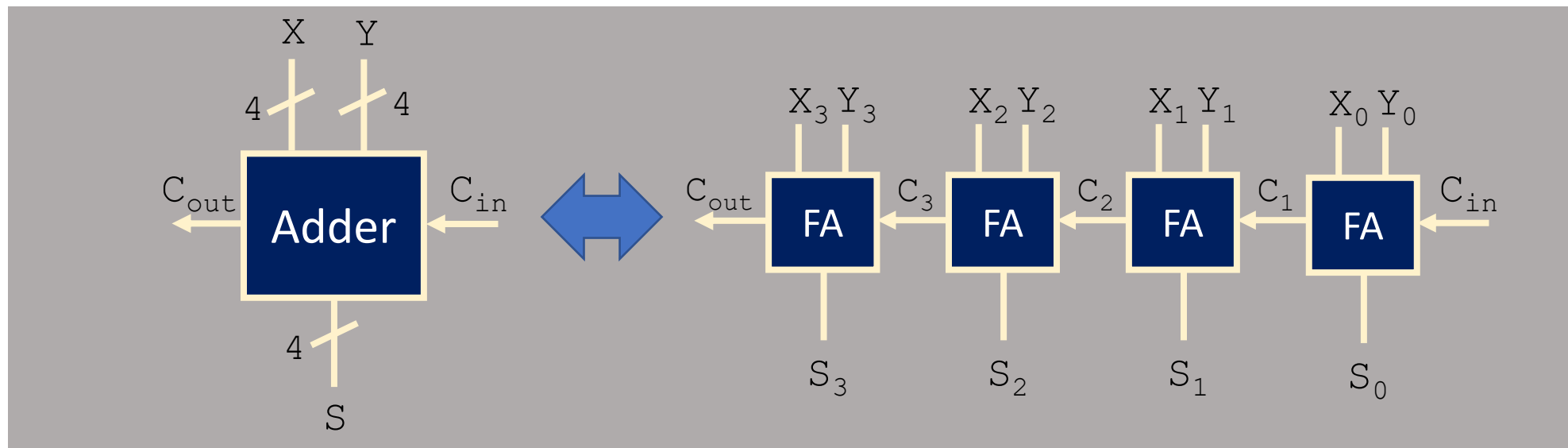
- Full adder units are chained together in order to perform operations on signal **vectors**.



$S_3S_2S_1S_0$ is the sum of $X_3X_2X_1X_0$ and $Y_3Y_2Y_1Y_0$

The role of C_{in}

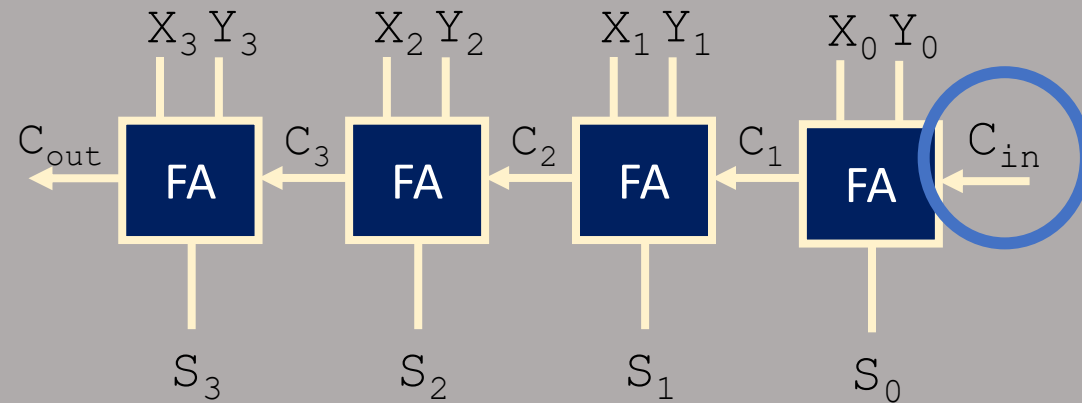- Why can't we just have a half-adder for the smallest (right-most) bit?
- Because if we can use it to do **subtraction**!



Let's play a game...

1. Pick two numbers between 0 and 31
2. Convert both numbers to **5-bit** binary form
- 3. Invert** each digit of the **smaller** number
4. Add up the big binary number and the inverted small binary number
- 5. Add 1** to the result, keep the lowest 5 digits
6. Convert the result to a decimal number

What do you get?

You just did subtraction
without doing subtraction!

Subtractors

- Subtractors are an extension of adders.
 - Basically, perform addition on a negative number.
- Before we can do subtraction, need to understand negative binary numbers.
- Two types:
 - **Unsigned** = a separate bit exists for the sign; data bits store the positive version of the number.
 - **Signed** = all bits are used to store a **2's complement** negative number.

Two's complement

- Need to know how to get **1's complement**:
 - Given number X with n bits, take $(2^n - 1) - X$
 - Negates each individual bit (bitwise NOT).

01001101	→	10110010
11111111	→	00000000

- **2's complement** = (1's complement + 1)

01001101	→	10110011
11111111	→	00000001

} Know this!

- Note: Adding a 2's complement number to the original number produces a result of zero.

(2's complement of A) + A = 0.

The 2's complement of A is like -A

Unsigned subtraction (separate sign bit)

- General algorithm for **A - B**:
 1. Get the **2's complement** of **B** (-B)
 2. Add that value to **A**
 3. If there is an end carry (C_{out} is high), the final result is positive and does not change.
 4. If there is no end carry (C_{out} is low), get the 2's complement of the result (B-A) and add a **negative sign** to it, or set the sign bit high ($-(B-A) = A-B$).

Unsigned subtraction example

• $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



$$\begin{array}{r} 00110101 \\ +11100101 \\ \hline \end{array}$$

carry bit

$$\begin{array}{r} 100011010 \end{array}$$



$$\boxed{00011010}$$

carry bit is high
(positive)

26

• $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



$$\begin{array}{r} 00011011 \\ +11001011 \\ \hline \end{array}$$

no carry bit

$$\begin{array}{r} 011100110 \end{array}$$



$$\boxed{-00011010}$$

carry bit is low
(negative)

2's complement

-26

Signed subtraction (easier)

- Store negative numbers in 2's complement notation.
 - Subtraction can then be performed by using the binary **adder** circuit with negative numbers.
 - To compute $A - B$, just do $A + (-B)$
 - Need to get $-B$ first (the 2's complement of B)

Signed subtraction example (6-bit)

- $21 - 23$
- 23 is 010111
- 21 is 010101
- -23 is 101001 (2's complement of 32)
- $21 - 23$ is 111110 which is -2

Signed addition example (6-bit)

- $21 + 23$
- 23 is 010111
- 21 is 010101
- $23+21$: 101100
- This is -20!
- The supposed result 44 is exceeding the range of 6-bit signed integers. This is called an overflow.

Now you understand C code better

```
#include <stdio.h>

int main()
{
    /* char is 8-bit integer */
    signed char a = 100;
    signed char b = 120;
    signed char s = a + b;
    printf("%d\n", s);
}
```


Trivia about sign numbers

- The **largest positive** 8-bit signed integer?
 - $01111111 = 127$ (0 followed by all 1)
- The **smallest negative** 8-bit signed integer?
 - $10000000 = -128$ (1 followed by all 0)
- The binary form 8-bit signed integer **-1**?
 - 11111111 (all one)
- For n-bit signed number there are 2^n possible values
 - 2^{n-1} are negative numbers (e.g. 8 bit, -1 to -128)
 - $2^{n-1}-1$ are positive number (e.g. 8 bit, 1 to 127)
 - and a zero



-128: 10000000 (signed)

Subtraction circuit

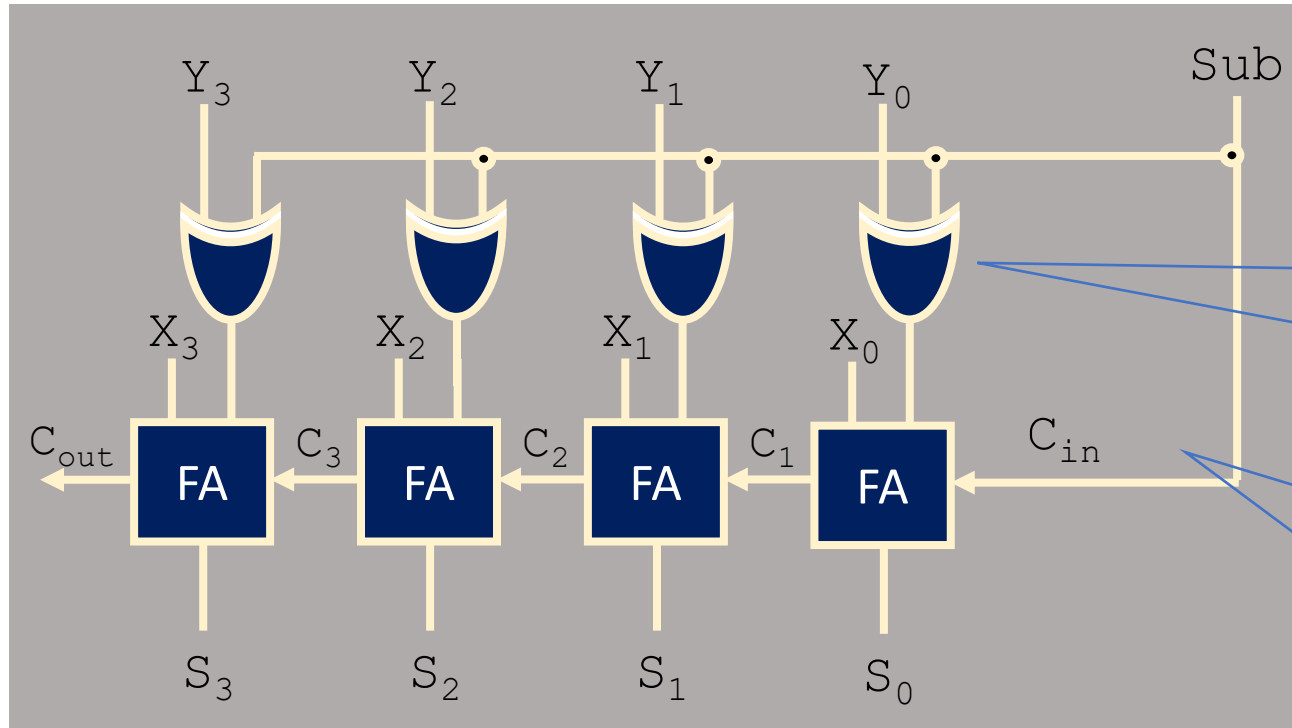

Invert all the digits (if sub = 1)

Add 1, so getting 2's complement

- If $\text{sub} = 0$, $S = X + Y$
- If $\text{sub} = 1$, $S = X - Y$


One circuit, both adder or subtractor



Decoders




What is a decoder?

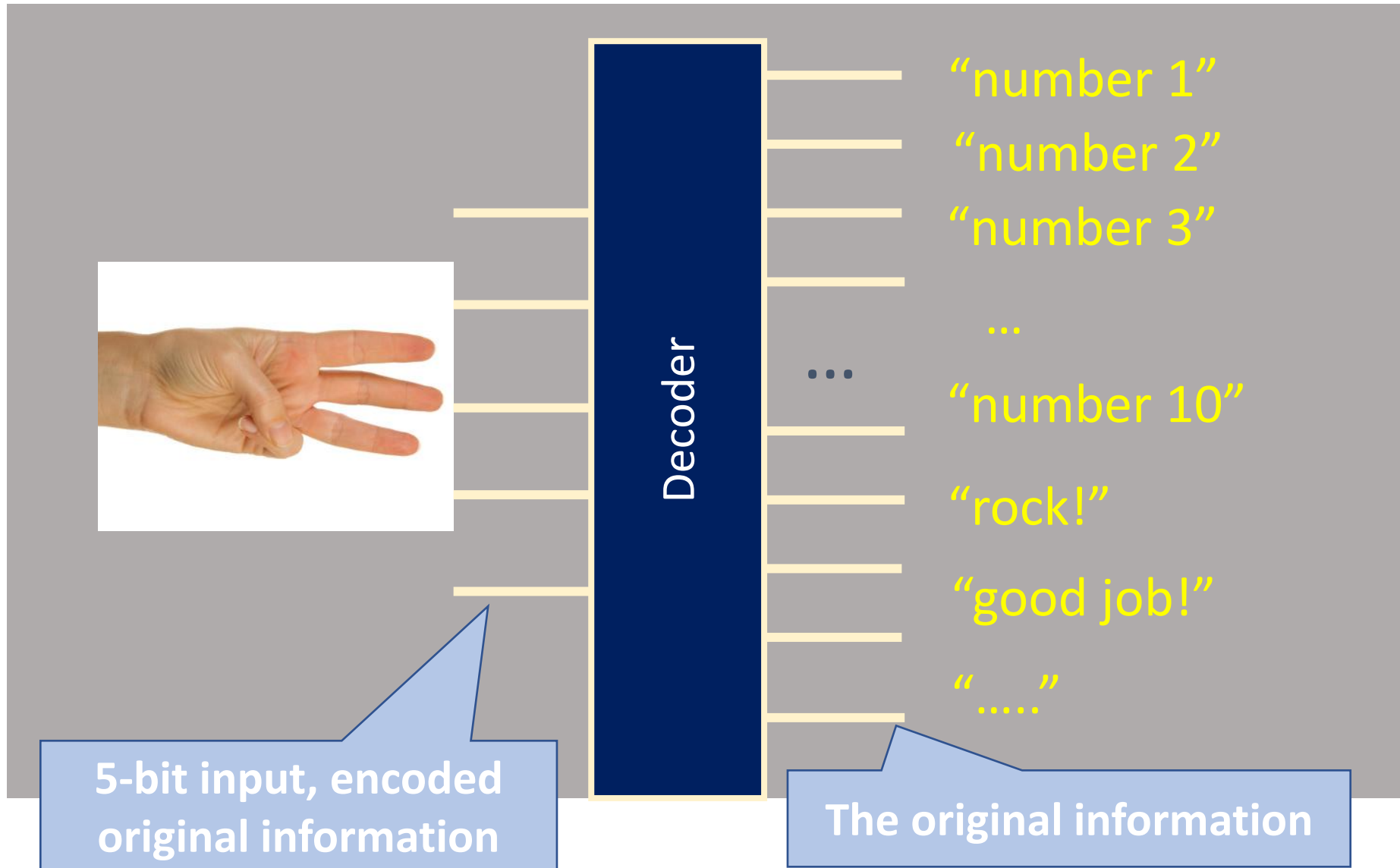


Decoders

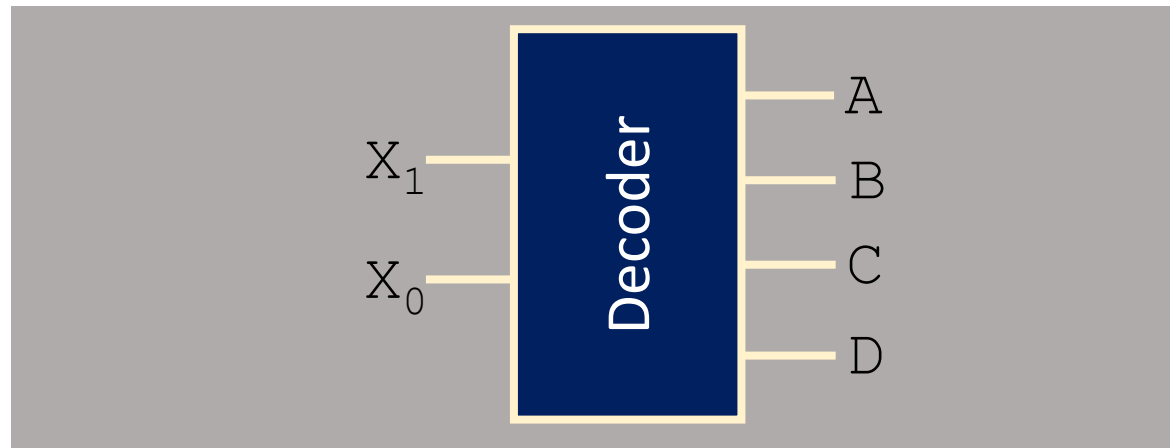- Decoders are essentially translators.
 - Translate from the output of one circuit to the input of another.
- Example: Binary signal splitter
 - Activates one of four output lines, based on a two-digit binary number.



Demultiplexers

 - Related to decoders: demultiplexers.
 - Does multiplexer operation, in reverse.




Multiplexer:

Choose one from multiple inputs as output


Demultiplexer:

One input chooses from multiple outputs

7-segment decoder

 

 - Common and useful decoder application.
 - Translate from a 4-digit binary number to the seven segments of a digital display.
 - Each output segment has a particular logic that defines it.
 - Example: Segment 0
 - Activate for values: 0, 2, 3, 5, 6, 7, 8, 9.
 - In binary: 0000, 0010, 0011, 0101, 0110, 0111, 1000, 1001.
 - First step: Build the truth table and K-map.




Note

What we talk about here is NOT the same as what we do in Lab 2

- In labs we translate numbers 0, 1, 3, 4, 5, 6 to displayed letters such as (H, E, L, L, O, _, E, L, I)
 - This is specially defined for the lab
- Here we are talking about translating 0, 1, 2, 3, 4,..., to displayed 0, 1, 2, 3, 4, ...
 - This is more common use

7-segment decoder

- For 7-seg decoders, turning a segment on involves driving it low. (active low)
 - (In Lab 2, we treat it like active high. It's OK because Logisim does auto-conversion to make it work).
 - i.e. Assuming a 4-digit binary number, segment 0 is low whenever input number is 0000, 0010, 0011, 0101, 0110, 0111, 1000 or 1001, and high whenever input number is 0001 or 0100.
 - This create a truth table and map like the following...

 


7-segment decoder

x_3	x_2	x_1	x_0	HEX ₀
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

6 rows missing!
1010 ~ 1111

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

 - $HEX_0 = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$
- But what about input values from 1010 to 1111?



“Don’t care” values


- Some input values will never happen, so their output values do not have to be defined.
 - Recorded as ‘X’ in the Karnaugh map.
- These values can be assigned to whatever values you want, when constructing the final circuit.

$$\text{HEX0} = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 \\ + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$$

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$	X	X	X	X
$x_3 \cdot \bar{x}_2$	0	0	X	X

Boxes can cover “x”s, or not, whichever you like.

Again for segment 1

 


x_3	x_2	x_1	x_0	HEX ₁
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	0
$\bar{x}_3 \cdot x_2$	0	1	0	1
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX1} = x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0$$

Again for segment 2

 


x_3	x_2	x_1	x_0	HEX ₂
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	1
$\bar{x}_3 \cdot x_2$	0	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX2} = \bar{x}_2 \cdot x_1 \cdot \bar{x}_0$$

The final 7-seg decoder

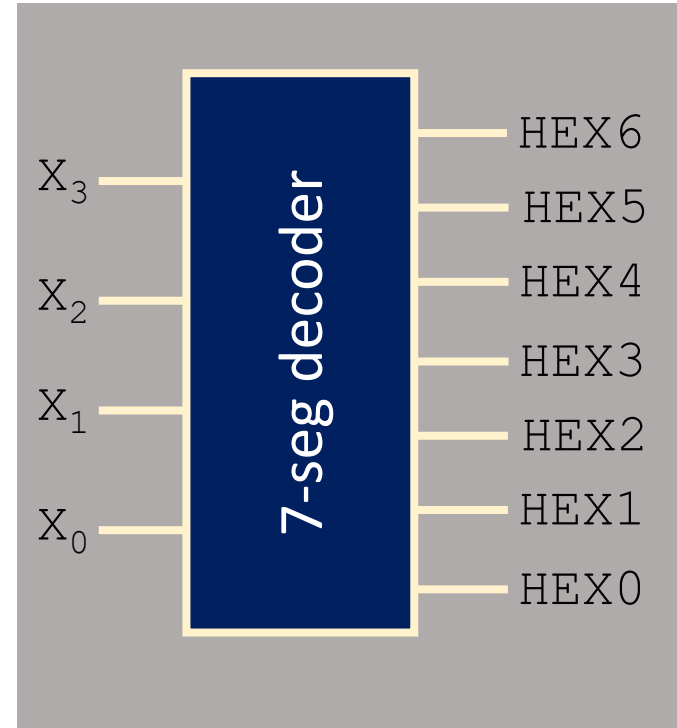- Decoders all look the same, except for the inputs and outputs.
- Unlike other devices, the implementation differs from decoder to decoder.



Comparators



Comparators

- A circuit that takes in two input vectors, and determines if the first is greater than, less than or equal to the second.
- How does one make that in a circuit?



Basic Comparators

- Consider two binary numbers A and B, where A and B are one bit long.
- The circuits for this would be:

- $A=B$:


$$A \cdot B + \bar{A} \cdot \bar{B}$$

- $A>B$:

$$A \cdot \bar{B}$$

- $A<B$:


$$\bar{A} \cdot B$$

 

A	B
0	0
0	1
1	0
1	1

Basic Comparators

 - What if A and B are two bits long?
- The terms for this circuit for have to expand to reflect the second signal.
- For example:



- $A==B$:


$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

Make sure that the values
of bit 1 are the same

Make sure that the values
of bit 0 are the same

Basic Comparators

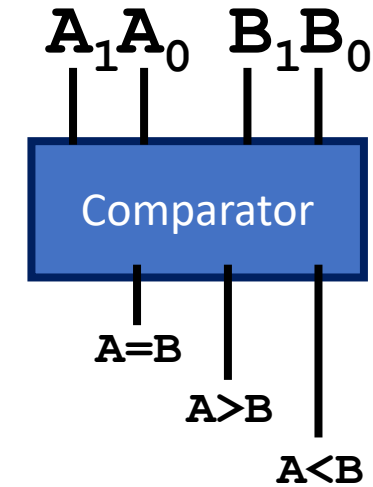- What about checking if A is greater than B?



- $A > B$:

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$


Check if first bit satisfies condition



If not, check that the first bits are equal...



...and then do the 1-bit comparison

 

- $A < B$:

$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$

$A > B$ if and only if $A_1 > B_1$ or $(A_1 = B_1$ and $A_0 > B_0)$

General Comparators

- The general circuit for comparators requires you to define equations for each case.
- Case #1: Equality
 - If inputs A and B are equal, then all bits must be the same.

- Define X_i for any digit i :
 - (equality for digit i)

$$X_i = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i$$

- Equality between A and B is defined as:

$$A==B : X_0 \cdot X_1 \cdot \dots \cdot X_n$$

Comparators

- Case #2: $A > B$
 - The first non-matching bits occur at bit i , where $A_i=1$ and $B_i=0$. All higher bits match.
 - Using the definition for X_i from before:

$$A > B = A_n \cdot \bar{B}_n + X_n \cdot A_{n-1} \cdot \bar{B}_{n-1} + \dots + A_0 \cdot \bar{B}_0 \cdot \prod_{k=1}^n X_k$$

- Case #3: $A < B$
 - The first non-matching bits occur at bit i , where $A_i=0$ and $B_i=1$. Again, all higher bits match.

$$A < B = \bar{A}_n \cdot B_n + X_n \cdot \bar{A}_{n-1} \cdot B_{n-1} + \dots + \bar{A}_0 \cdot B_0 \cdot \prod_{k=1}^n X_k$$

Comparator truth table

- Given two input vectors of size $n=2$, output of circuit is shown at right.

Inputs				Outputs		
A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Comparator example (cont'd)

$A < B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	1	1	1
$A_0 \cdot \bar{A}_1$	0	0	1	1
$A_0 \cdot A_1$	0	0	0	0
$\bar{A}_0 \cdot A_1$	0	0	1	0

$$LT = B_1 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot \bar{A}_0 + B_0 \cdot \bar{A}_0 \cdot \bar{A}_1$$

Comparator example (cont'd)

$A=B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot \bar{A}_1$	0	1	0	0
$A_0 \cdot A_1$	0	0	1	0
$\bar{A}_0 \cdot A_1$	0	0	0	1

$$EQ = \bar{B}_0 \cdot \bar{B}_1 \cdot \bar{A}_0 \cdot \bar{A}_1 + B_0 \cdot \bar{B}_1 \cdot A_0 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot A_0 \cdot A_1 + \bar{B}_0 \cdot B_1 \cdot \bar{A}_0 \cdot A_1$$

Comparator example (cont'd)


$A > B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	0	0	0
$A_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot A_1$	1	1	0	1
$\bar{A}_0 \cdot A_1$	1	1	0	0

$$GT = \bar{B}_1 \cdot A_1 + \bar{B}_0 \cdot \bar{B}_1 \cdot A_0 + \bar{B}_0 \cdot A_0 \cdot A_1$$

Comparing larger numbers

 - As numbers get larger, the comparator circuit gets more complex.
- At a certain level, it can be easier sometimes to just process the result of a subtraction operation instead.
 - Easier, less circuitry, just not faster.



Today we learned


How a computer does following things

- Control the flow of signal (mux and demux)
- Arithmetic operations: adder, subtractor
- Decoder
- Comparators

Next week:

- Sequential circuits: circuits that have **memories**.


CSCB58: Computer Organization

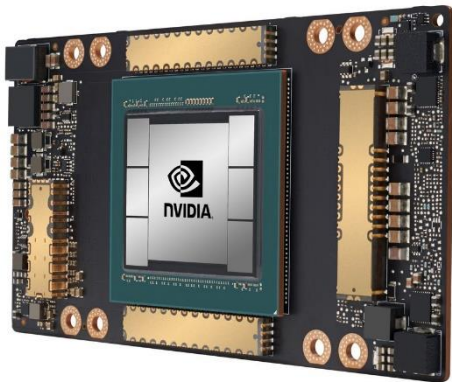

Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

 

*The content of this lecture is adapted from the lectures of
Larry Zheng and Steve Engels*